

Fall 2016 – CS2420

Homework 6

Due Date : Monday - November 16th , 2016 - Class Time


1) Design a combination logic circuit that counts the number of 1's present in 3 inputs A, B and C. Its output is a two-bit number X_1X_0 , representing that count in binary (15 pts.).

a) Write the truth table for this circuit.

b) Using a K-Map , find the minimized logic equations for outputs X_1 and X_0

c) Draw the corresponding logic diagram for this circuit. Label all inputs and outputs.

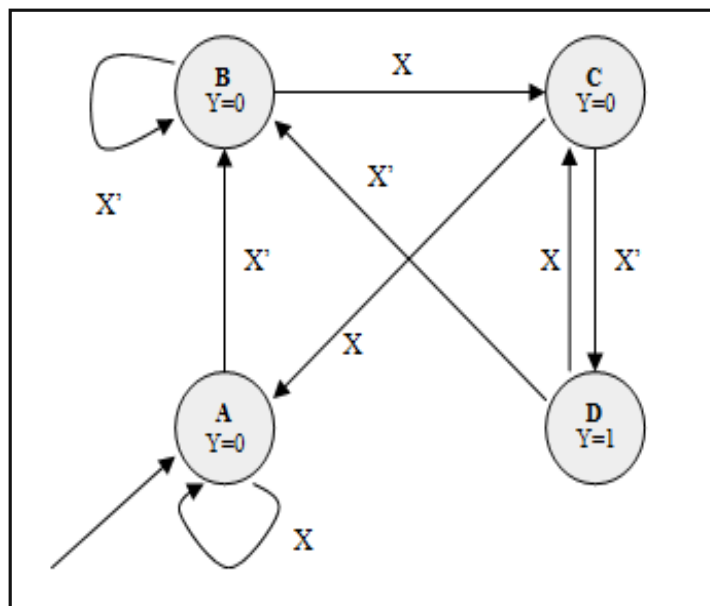2) We want to design a complete sequential circuit for a sequence detector which can detect a sequence of 010 on its input X. When this sequence if detected , the output Y will be equal to 1 for exactly one clock cycle. The Finite state machine is as follows (20 points) :



4) Using Mealy Model , design a complete sequential circuit for the following candy machine (25 pts.):

- The machine Release item after 15 cents are deposited
- The machine has a Single coin slot for dimes, nickels
- The machine will not return any changes back.

Your solution must include the following :-

- Finite state diagram
- Input / Output
- Finite state transition table
- Function equations
- Sequential logic circuit

Remarks :

- The homework does not have to be typed , however , it must be written using **pencils** only . Include the following information on **the top left** hand side of the first page :-
 - Your Name :
 - Your Roster or Serial Number :
 - Homework Number : 6
 - Due Date : November 16th , 2016
- **Make sure that you write the question first then followed by your answer.**
- The homework must also be uploaded using homework upload no later than the end of class time on the due date. Use the following name format for your file name
**LastName_FirstName_CS2420-A6.zip or
LastName_FirstName_CS2420-A6.pdf or
LastName_FirstName_CS2420-A6.doc**
- For each question , you must **show** all your work.
- **Missing ANY of the above items from your assignment will result in deducting 15 % of the assignment grade. NO EXCEPTIONS.**

Turn in hard copy of your assignment no later no than the end of class time on the due date. The hard copy must be **stapled**. **No Late assignment will be accepted and a grade of zero will be assigned.** If you are absent on the assignment's due date , a grade of zero will be recorded .

- **Copying the assignment from others will result in grade ZERO.**