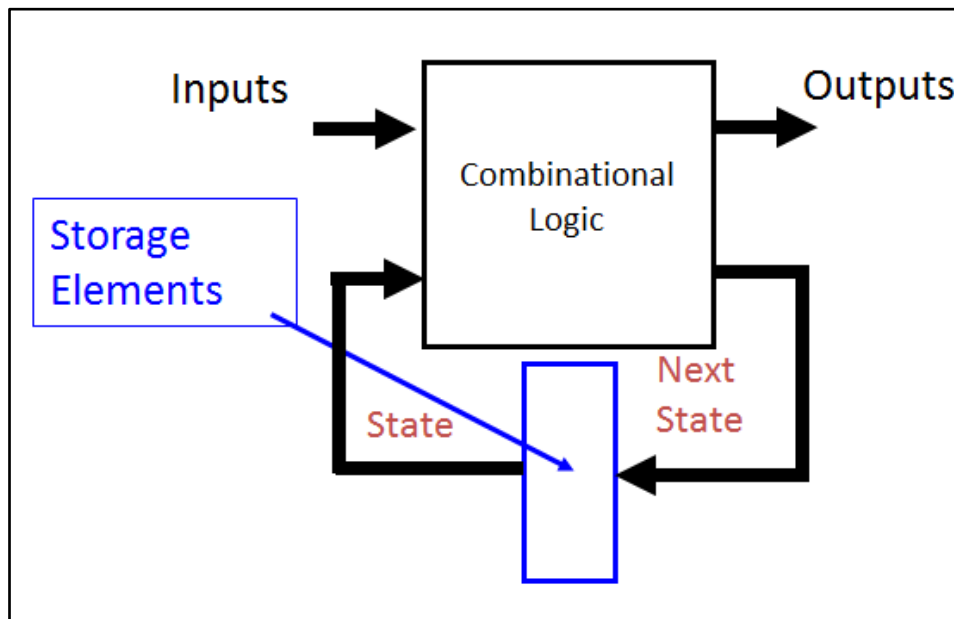


## Outline


- sequential circuits
- storage elements: latch and flip-flop
  
- Sequential circuit analysis
  - *Moore and Mealy Models*
  - *State tables*
  - *State diagrams*

## Introduction to Sequential Circuits

- A Sequential circuit contains:
  - Storage elements:  
Latches or Flip-Flops
  - Combinational Logic:
    - **Implements a multiple-output switching function**
    - Signals from the outside are **inputs**.
    - Signals to the outside are **outputs**.
    - **Other inputs**, State or Present State, are signals from storage elements.
    - **The remaining outputs**, Next State are inputs to storage elements.



- Combinatorial Logic

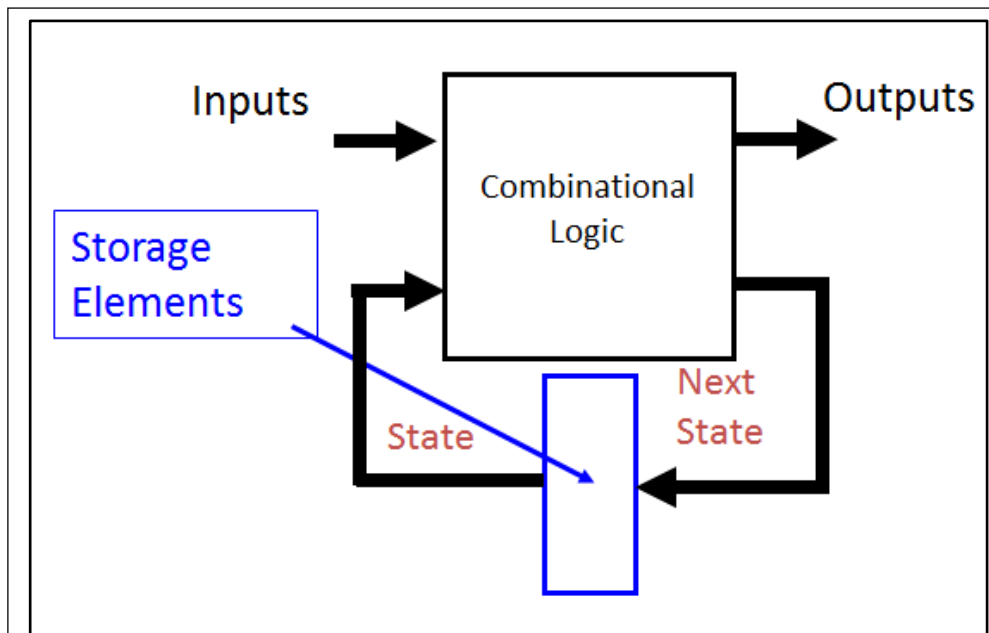

- *Next state function*  
Next State =  $f(\text{Inputs}, \text{State})$
- *Output is a function of inputs and State.*


## Storage element

- **Storage elements:** devices capable of storing binary information

**flip-flop:** used in clocked sequential circuit, storing one bit of information: state

The flip-flop is updated when a pulse of the clock signal occurs.


**Latch:** basic component of flip-flop.

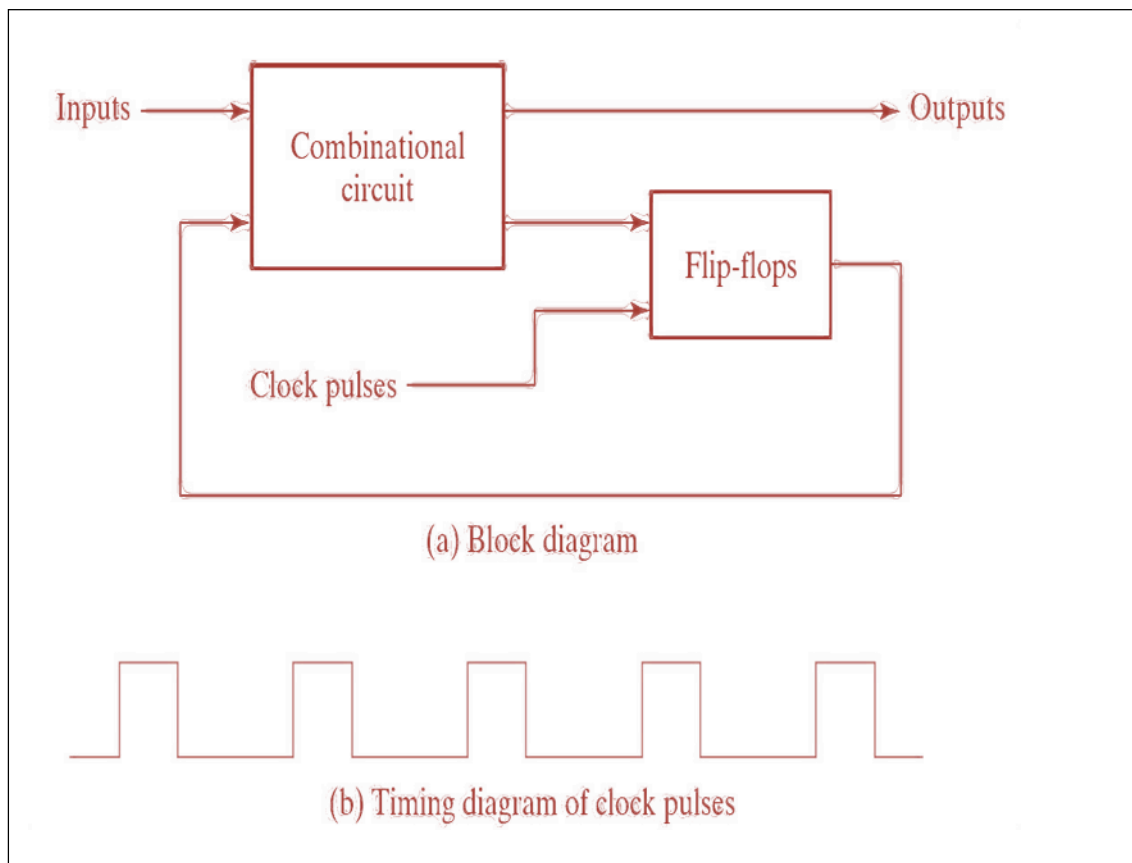


## Basic (NAND) S – R ( [Set-Reset latch](#) )Latch

- “Cross-Coupling” two NAND gates gives the S' -R' ( Set – Reset ) Latch:

Which has the time sequence behavior:

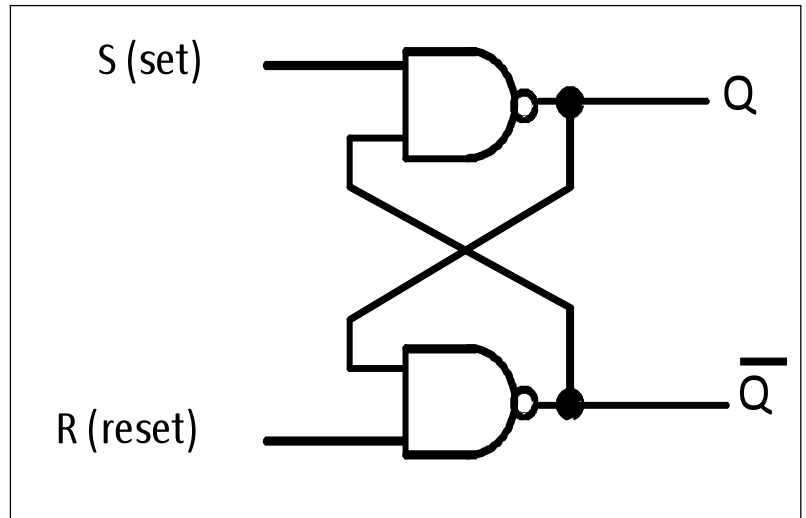


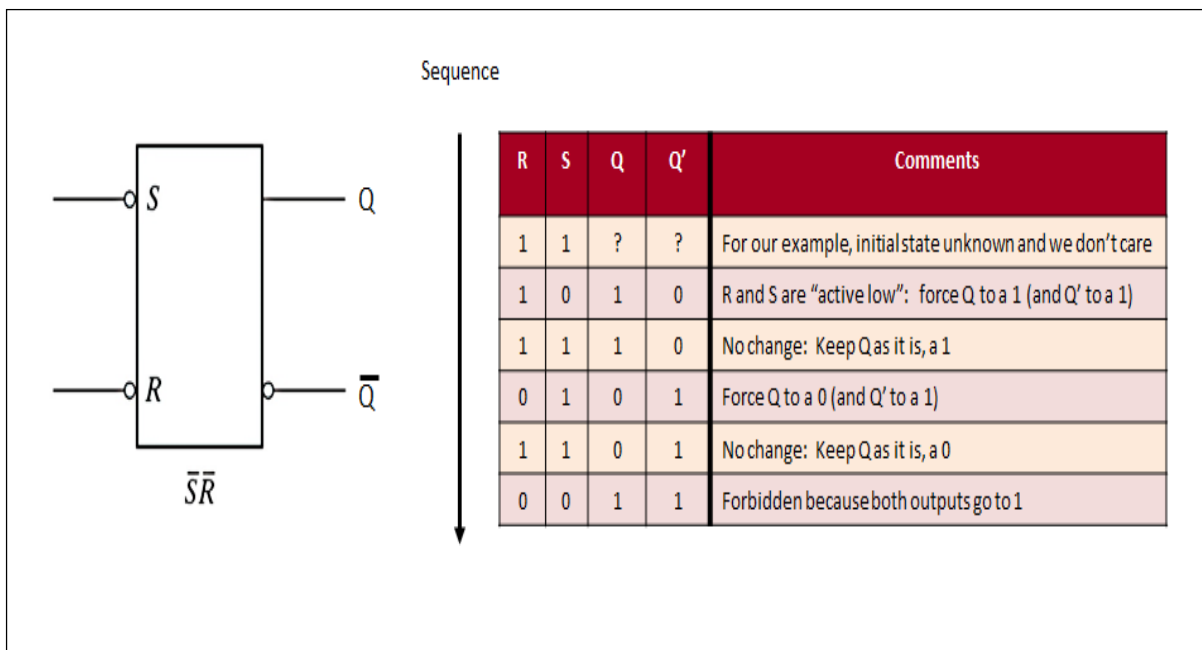S = 0, R = 0 is forbidden as input pattern



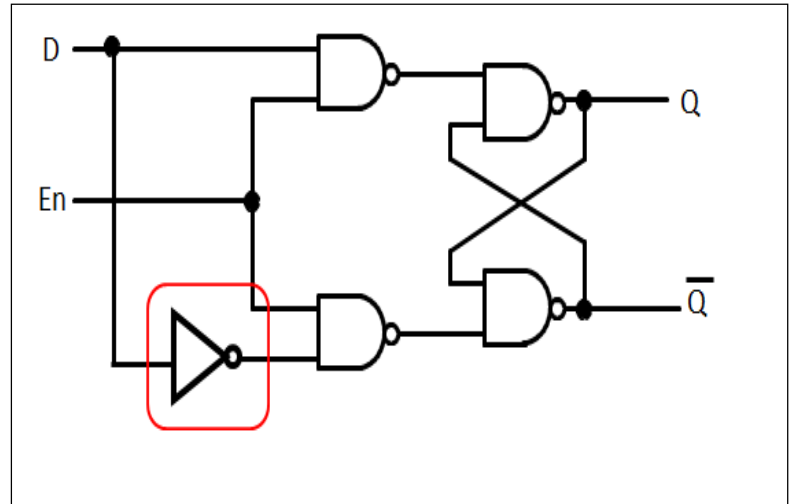
## D Latch

- Adding an inverter to the S-R Latch, gives the D Latch




(shown with an enable input)

The graphic symbol for a D Latch is:

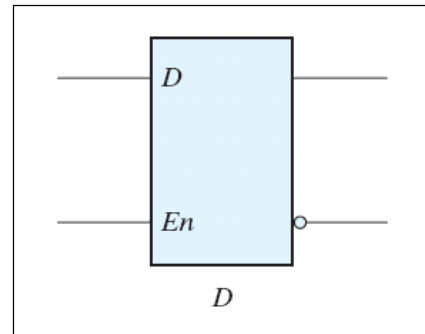


The enable input often acts as the clock.

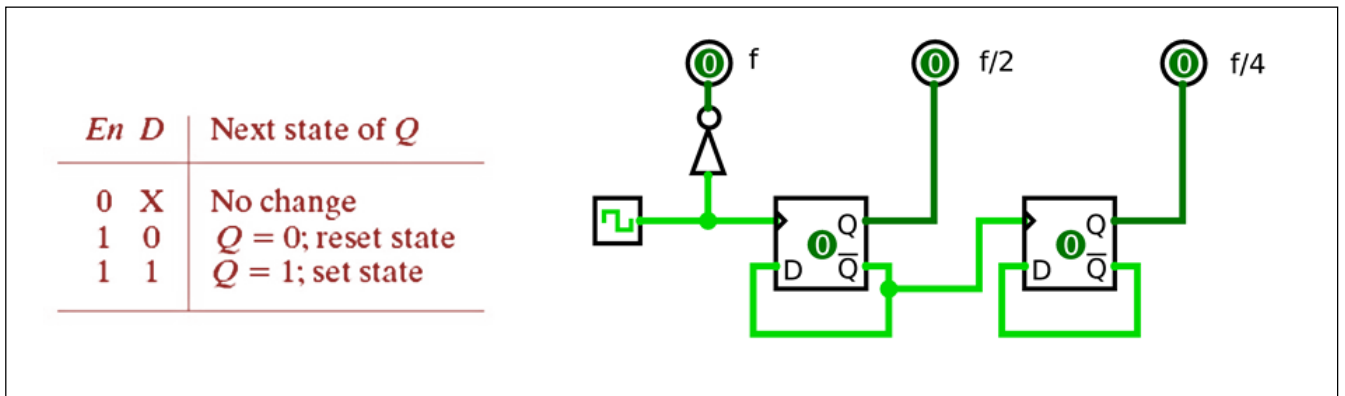- Note that there are no “indeterminate” states!



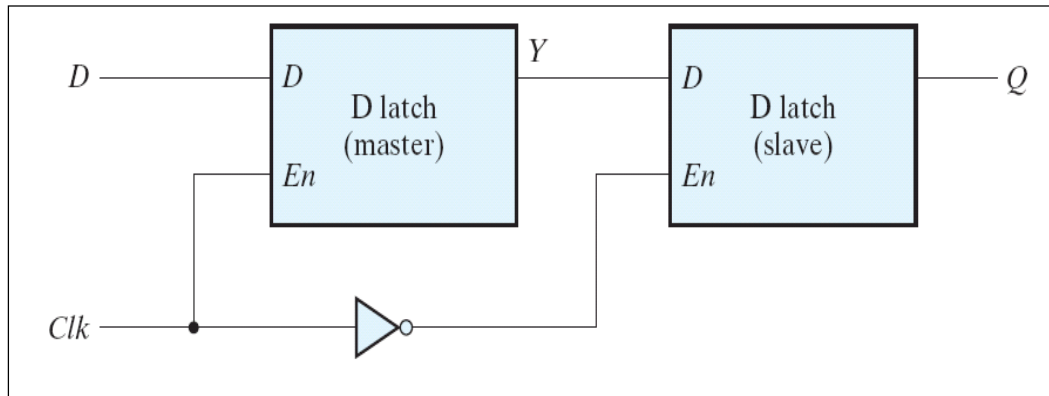
## Edge-Triggered D Flip-Flop

- The edge-triggered D flip-flop is the master-slave D flip-flop



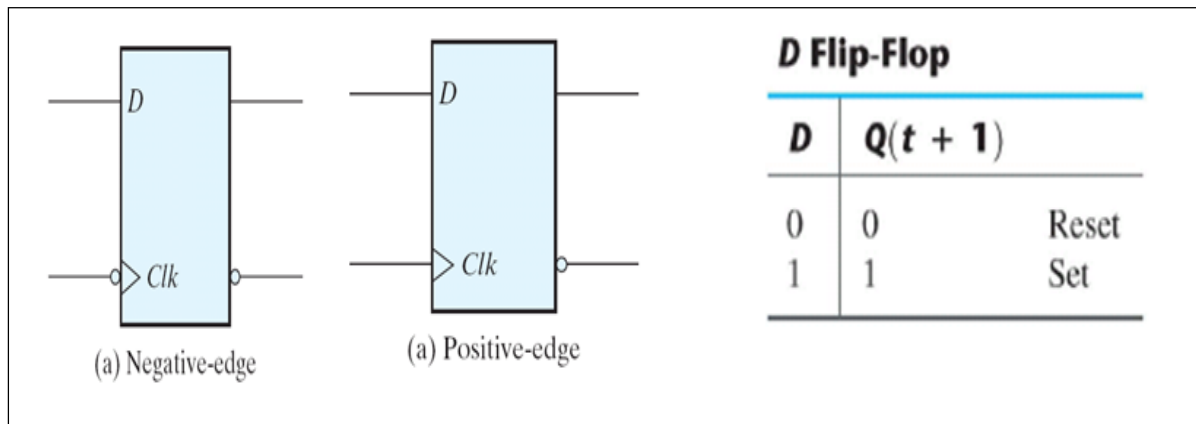
- The change of the D flip-flop output is associated with the negative (positive) edge at the end of the pulse


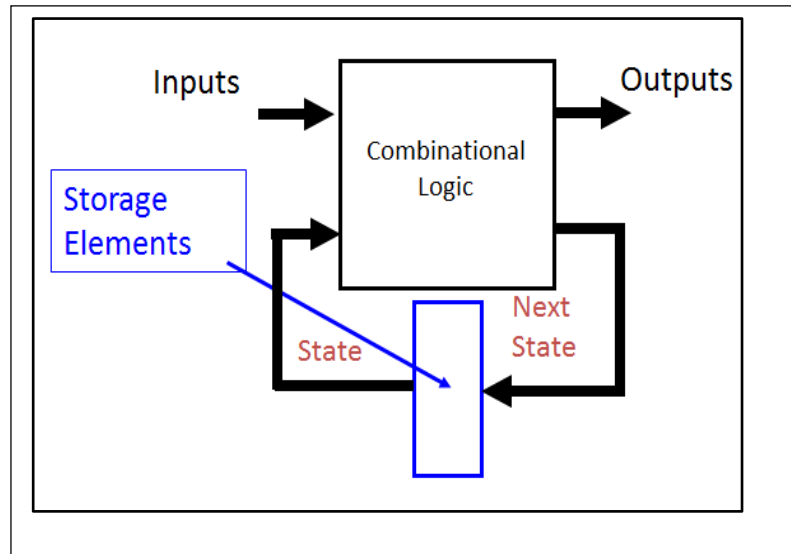
## Sequential Circuit Analysis

- General Model

- Current State at time (t) is stored in flip-flops.



- Next State at time (t+1) is a Boolean function of State and Inputs.
- Outputs at time (t) are a Boolean function of State (t) and (sometimes) Inputs (t).



## Moore and Mealy Models


- Sequential Circuits or Sequential Machines are also called *Finite State Machines* (FSMs). Two formal models exist:

### Mealy Model

- Named after G. Mealy
- Outputs are a function of inputs AND states

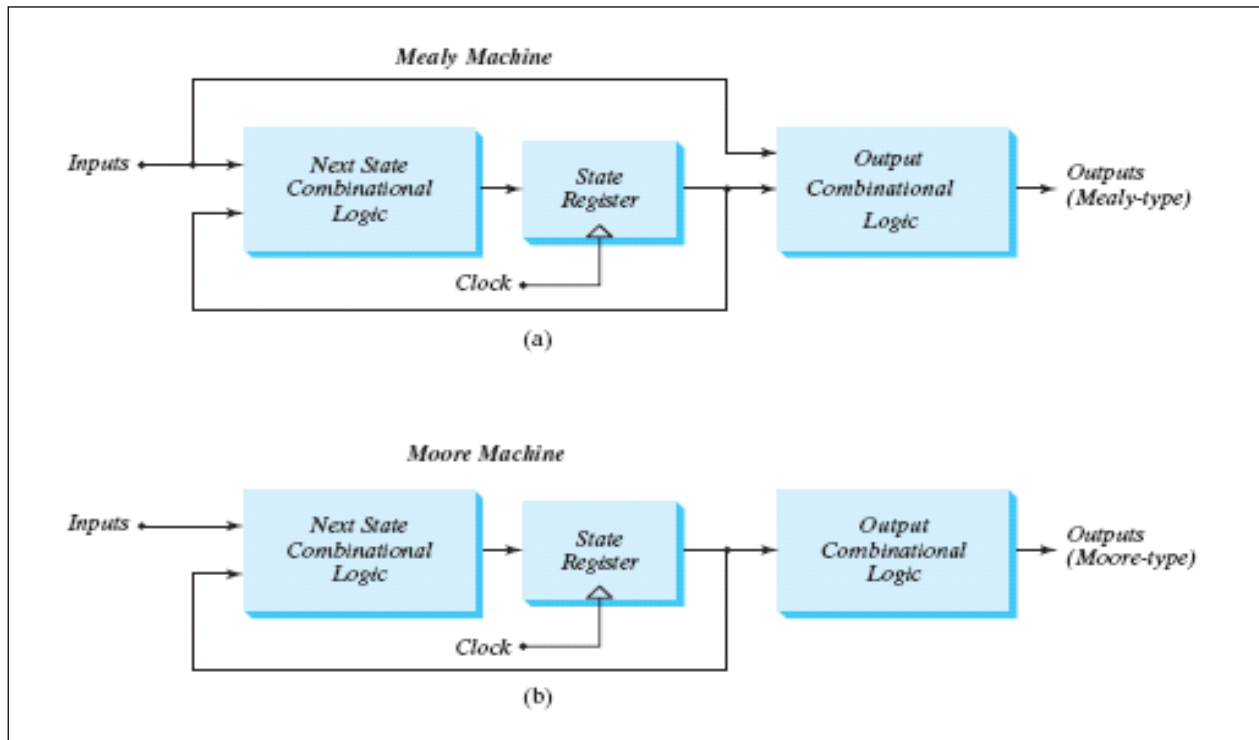
### Moore Model

- Named after E.F. Moore
- Outputs are a function ONLY of states


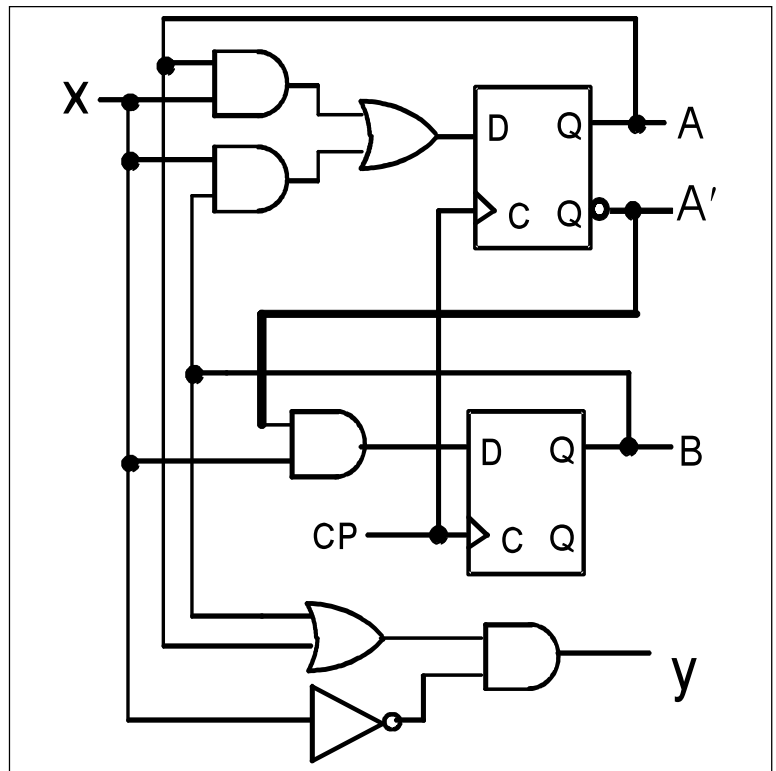
### Example 1

- Input:  $x$
- Output:  $y$
- State:  $(A, B)$
- What is the Output Function?
- What is the Next State Function?



- Mealy or Moore?

## Example 1 (continued)

### Step 1:

- Input flip-flop equations:

$$D_A = A'x + Bx$$

$$D_B = A'x$$

### Step 2:


- State equations:

$$A(t+1) = D_A = A'x + Bx$$

$$B(t+1) = D_B = A'x$$

Output equations:

$$y = x' (B + A)$$

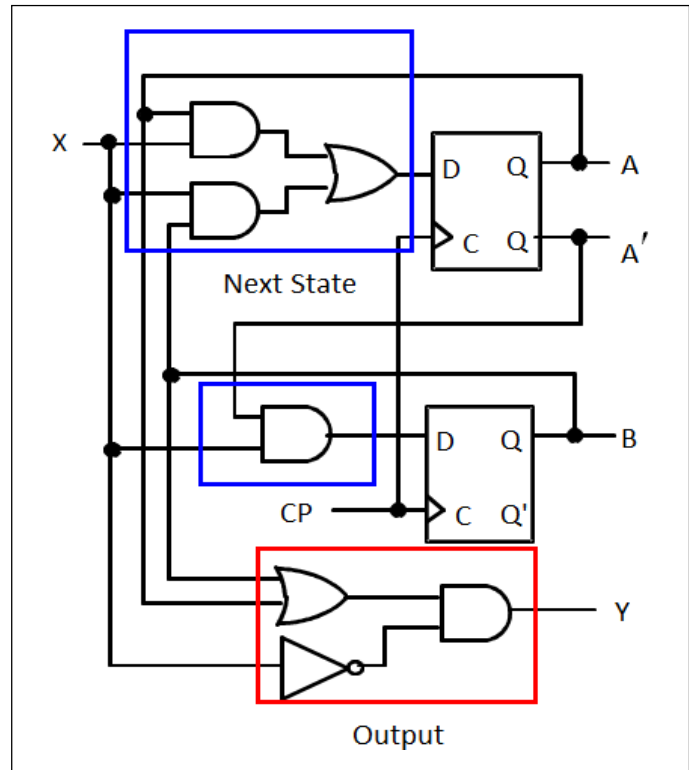

### Step 3:

- State Table and State Diagram

## State Table Characteristics

- *State table* – a multiple variable table with the following four sections:
  - ***Present State*** – the values of the state variables for each allowed state.
  - ***Input*** – the input combinations allowed.
  - ***Next-state*** – the value of the state at time (t+1) based on the present state and the input.
  - ***Output*** – the value of the output as a function of the present state and (sometimes) the input.
- Considered as a truth table:
  - the inputs are Input, Present State
  - and the outputs are Output, Next State


### Example1: State Table.

- The state table can be filled in using state equations and output equations:

$$A(t+1) = D_A = A(t)x(t) + B(t)x(t)$$

$$B(t+1) = D_B = A(t)'x(t)$$

$$y(t) = x(t)'(B(t) + A(t))$$

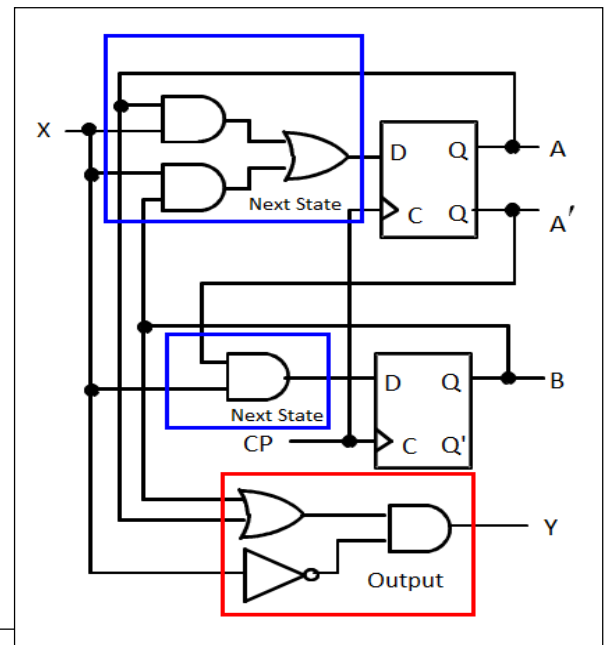

Present State		Input	Next State		Output
A(t)	B(t)		A(t+1)	B(t+1)	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0


## State Diagrams

- The sequential circuit function can be represented in graphical form as a state diagram with the following components:
  - A circle with the state name in it for each state
  - A directed arc from the Present State to the Next State for each state transition
  - A label on each directed arc with the Input values which causes the state transition, and
  - A label:
    - *On each directed arc with the output value produced (Mealy), or*
    - *On each circle with the output value produced (Moore)*

### Example 1: State Diagram


- On directed arc with the output included:
  - *input/output*
  - *Mealy type output depends on state and input*

Present State		Input	Next State		Output
$A_t$	$B_t$	$X_t$	$A_{t+1}$	$B_{t+1}$	$Y_t$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

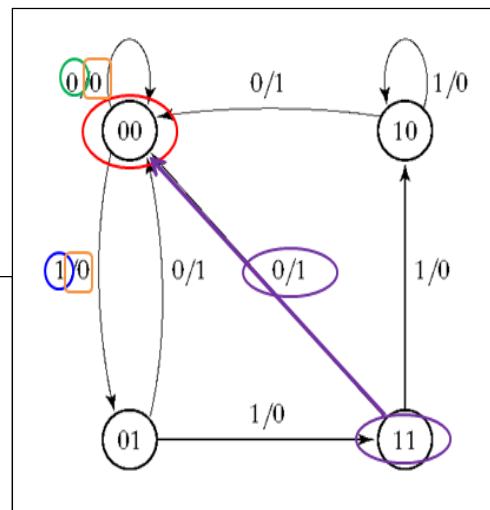
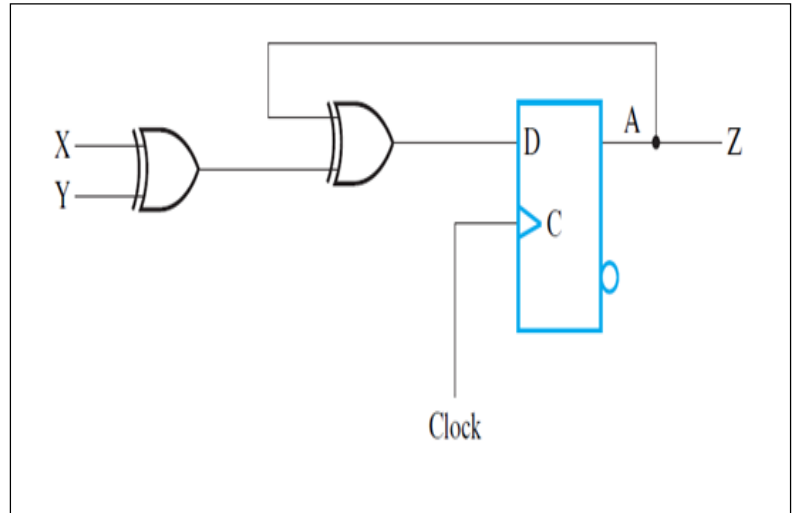
## Example 2

- Input:  $x, y$
- Output:  $Z$
- State:  $A$
- What is the Output Function?



- What is the Next State Function?

- Mealy or Moore?



## Example 2 (continued)

### Step 1:


- Input flip-flop equations:  
 $D_A = x \oplus y \oplus A$

### Step 2:

- State equations:  
 $A(t+1) = D_A = x \oplus y \oplus A$   
Output equations:  
 $Z(t) = A(t)$

### Step 3:

- State Table and State Diagram

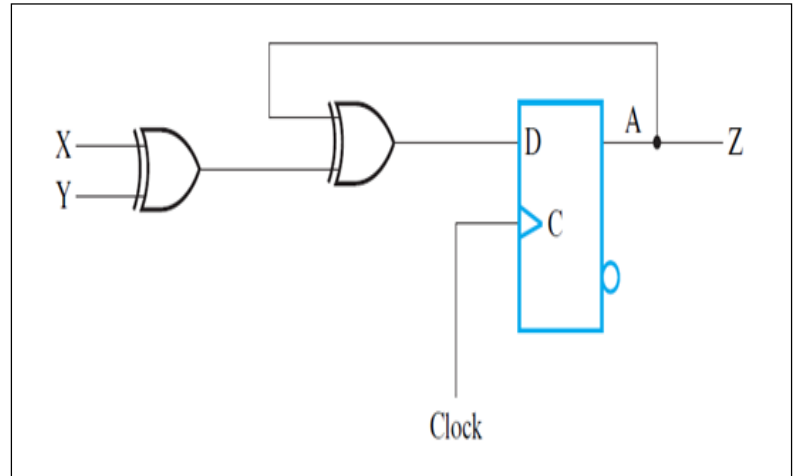


## Example2: State Table

- The state table can be filled in using state equations and output equation:

$$A(t+1) = D_A = x(t) \oplus y(t) \oplus A(t)$$


$$Z(t) = A(t)$$

Present state	Inputs		Next state	Output
A	X	Y	A	Z
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

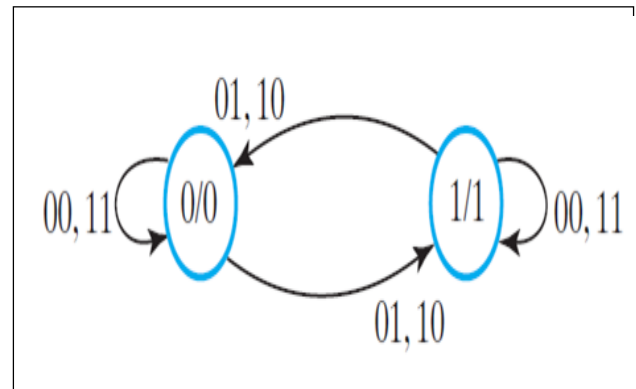
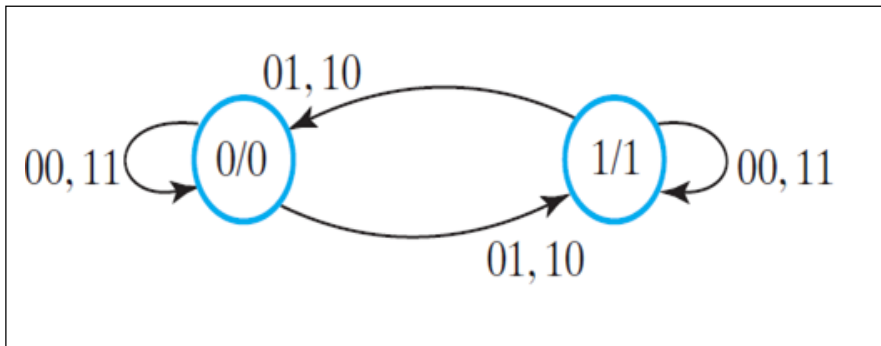
## Example 2: State Diagram

- On circle with output included:
  - *state/output*
  - *Moore type output depends only on state*



Present state	Inputs		Next state	Output
A	X	Y	A	Z
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1