 


Outline

- Classical CL circuits
 - **Decoder**
 - **Encoder**
 - **Multiplexer**


Decoder

Decoder – converts n -bit input lines to a maximum of 2^n unique output lines



n -to- m line decoders, where $n \leq m \leq 2^n$

 - Function: generate 2^n (or fewer) minterms for the n input variables



- 2-to-4-Line Decoder

Each line D_i is a minterm m_i


A_1	A_0	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

(a)

Decoder Examples

- 3-to-8-Line Decoder

Inputs			Outputs							
<i>x</i>	<i>y</i>	<i>z</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃	<i>D</i> ₄	<i>D</i> ₅	<i>D</i> ₆	<i>D</i> ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

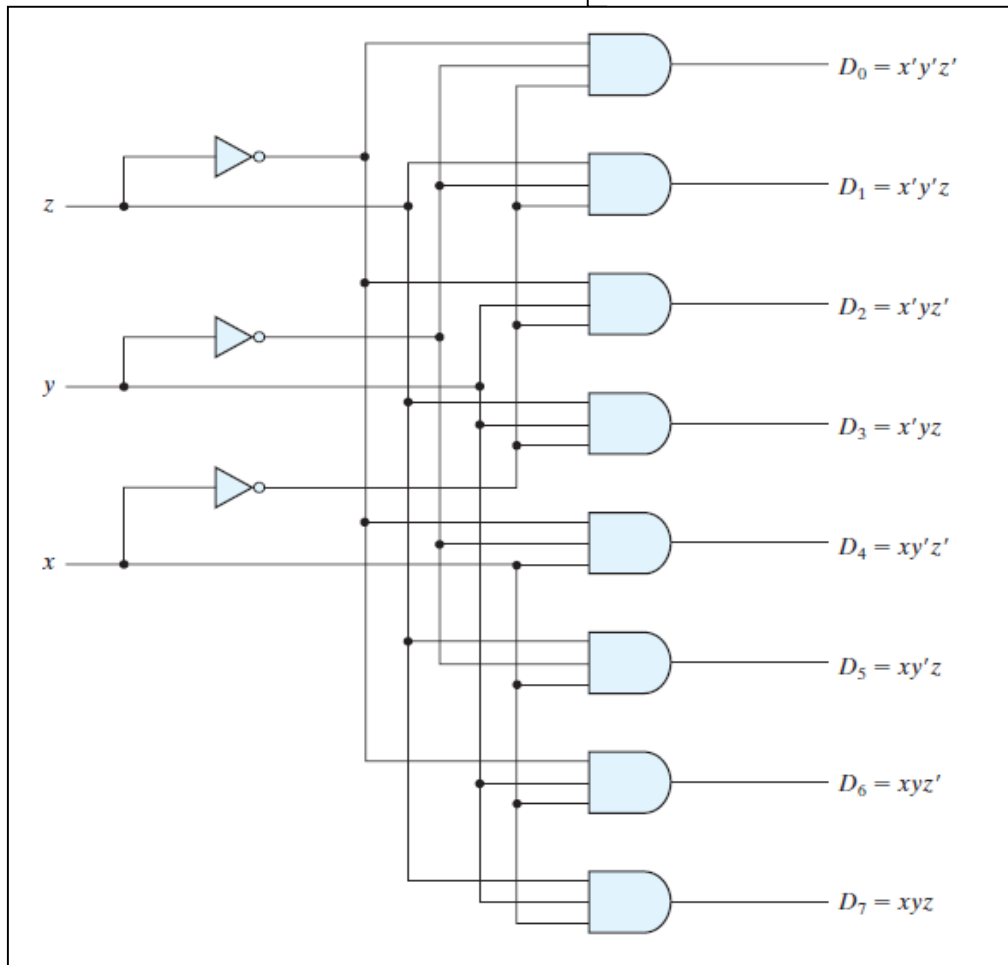


Application of Decoder

<i>Full Adder</i>				
x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S(x,y,z) = \sum(1,2,4,7)$$


$$C(x,y,z) = \sum(3,5,6,7)$$

 

Encoder

- Encoder- the opposite of decoding – convert m -bit input line to a n -bit unique output line

with $n \leq m \leq 2^n$

 

Encoder Example

- Inputs: 4 bits corresponding to decimal digits 0 through 3, (D_0, \dots, D_3)
- Outputs: 2 bits with binary codes
- Function: If input bit D_i is a 1, then the output (A_1, A_0) is the binary code for i

Input				Output	
D_3	D_2	D_1	D_0	A_1	A_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Input: 0 1 1 0 Output ?

Input: 0 0 0 0 Output ?


Priority Encoder

Among the 1s that appear, it selects the most significant input position (or the least significant input position) containing a 1 and responds with the corresponding binary code for that position.

Inputs				Outputs		
D_3	D_2	D_1	D_0	A_1	A_0	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1


Priority Encoder

Inputs				Outputs		
D ₃	D ₂	D ₁	D ₀	A ₁	A ₀	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

 

Priority Encoder
 
$$A_0 = D_3 + D_1 D_2' \quad A_1 = D_2 + D_3 \quad V = D_0 + D_1 + D_2 + D_3$$




Outline

- Analysis of Combinational Logic (CL)
- Design of CL
- Classical CL circuits
 - Adder
 - Subtractor
 - Comparator
 - Decoder
 - Encoder
 - Multiplexer

Multiplexer

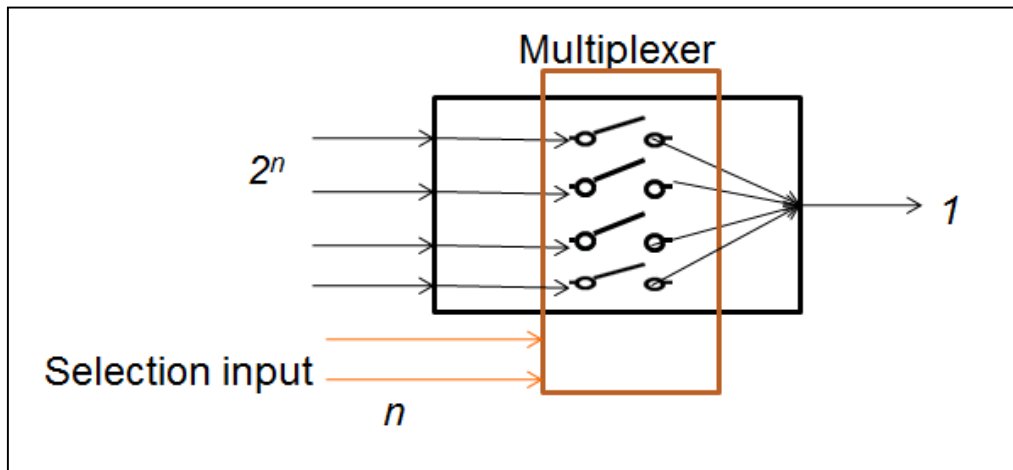
- A multiplexer selects binary information from **one** of many inputs and directs it to a **single** output line



- A typical multiplexer has n control inputs (S_{n-1}, \dots, S_0) called *selection inputs*, 2^n information inputs (I_{2^n-1}, \dots, I_0), and one output Y


Multiplexer

- 2-to-1-line multiplexer

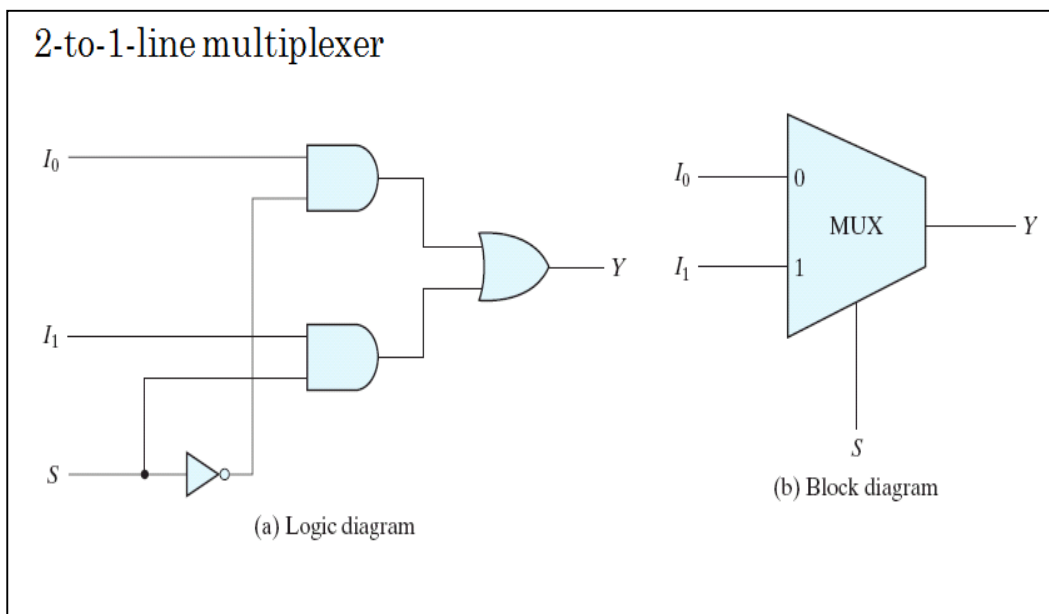

Multiplexer


- 4-to-1-line multiplexer

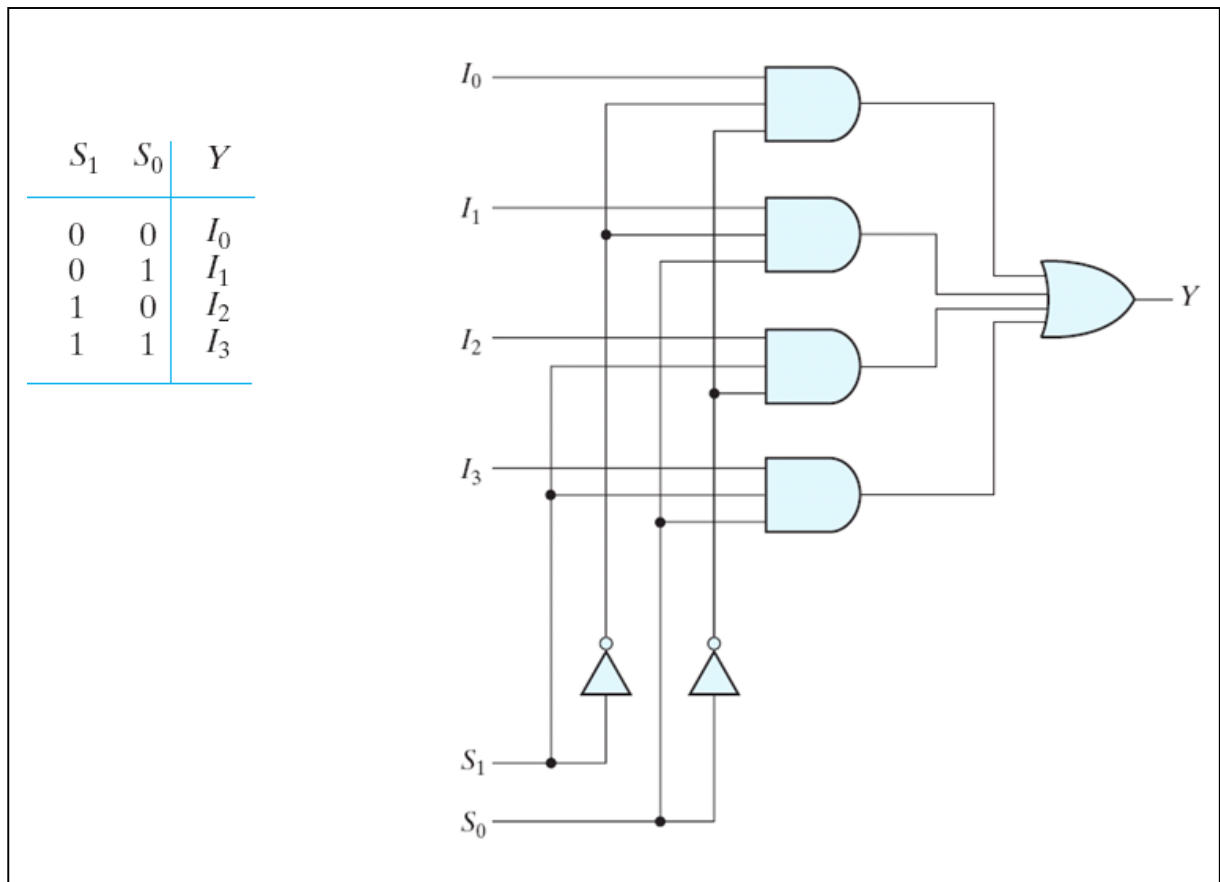

Multiplexer

In general, for an 2^n -to-1-line multiplexer:

 - 2^n data input
- n selection input
- 1 output
- n inverter
- 2^n AND gates
- 1 OR gate




Application of Multiplexer

- Implement Boolean function

$$F(x, y, z) = \sum(1, 2, 6, 7)$$

x	y	z	F	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	


(a) Truth table

 

Application of Multiplexer

$$F(A,B,C,D)=\Pi(0,2,5,6,7,8,9,10)$$

A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

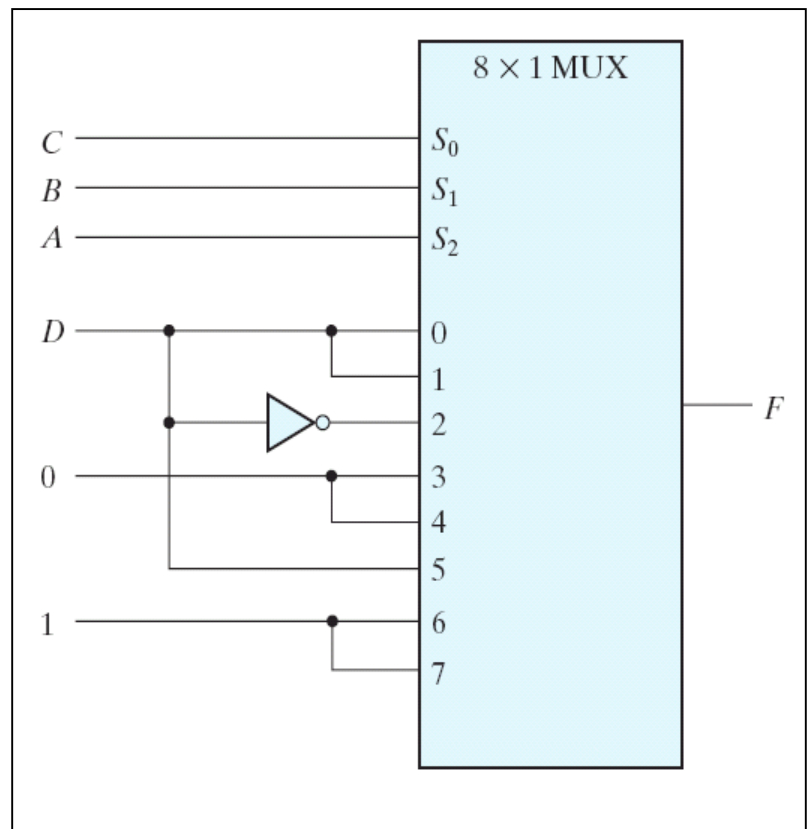

Construct a 8x1 multiplexer with two 4x1 and one 2x1 multiplexers. ?