

## Lecture 13 Chapter 7: Memory

### Overview

- Memory definitions
- Random Access Memory (RAM)
- Static RAM (SRAM) integrated circuits

### Memory Definitions

**Memory** – A storage device (a collection of storage cells) for read and write data

### Two types of memories:

- Random Access Memory (**RAM**)
  - Read and write at any time and any address
  - *Volatile* – loses stored information when power turned off
- Read-only Memory (**ROM**)
  - perform only read operation
  - *Non-volatile* – retains information when power turned off

## Memory Definitions

- Typical data elements are:
  - bit – a single binary digit
  - byte – a collection of eight bits accessed together
  - word
    - an entity of bits that move in and out of storage as a unit
    - typically multiple of 8 bits (bytes)
    - Example: 8-bit word, 16-bit word, 32-bit word

Capacity of a memory –usually stated as the total number of **bytes** that the unit can store

## MEMORY ORGANIZATION EXAMPLE

### Memory address:

- Value of the index for each word
  
- 16 bit per word  
 $1024=2^{10}$  words


Memory address		Memory content
Binary	Decimal	
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101

## Memory Block Diagram

- Data lines: input or output  
n-bit word: 8-bit, 16-bit, 32-bit
- Address bus:  
k address lines:  
--address space is  $2^k$  words  
--n bits per word  
 $2^k \times n$  memory

example: 64K x 10 memory

- Control:  
Read and Write  
Enable

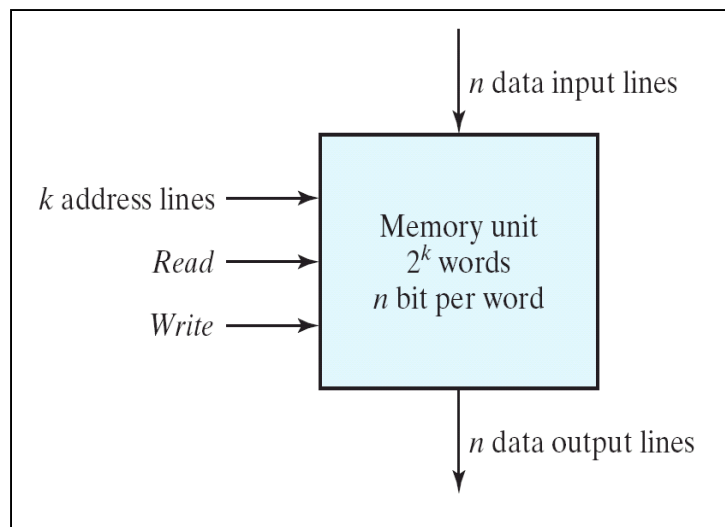

# RAM

## Data lines

- 16- bit

## Address lines

- 10- bit

So, it is a

- 1024×16 memory

Memory address		Memory content
Binary	Decimal	
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101

## Basic Memory Operations

### Write

- Apply the binary address of the desired word to the address lines
- Apply the data bits that to be stored in memory to the data input lines
- Activate write

### Read

- Apply the binary address of the desired word to the address lines
- Activate read

**Table 7.1**  
*Control Inputs to Memory Chip*

<b>Memory Enable</b>	<b>Read/Write</b>	<b>Memory Operation</b>
0	X	None
1	0	Write to selected word
1	1	Read from selected word


## Types of RAM

### Types of random access memory

- **SRAM: *Static*** – bits stored in latches and flipflops
- Information is valid as long as power is on
- Easier to use and faster to read and write

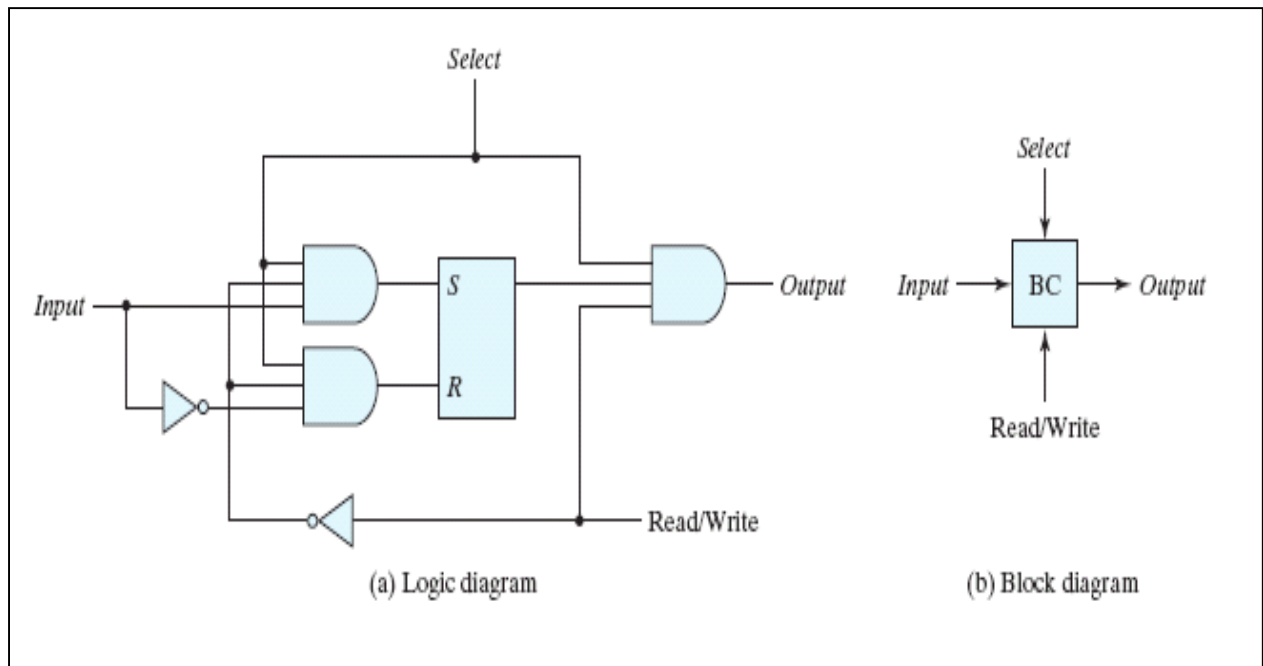
### Memory Cell

- If select=0, ???
- If select=1 and r/w=1, ???
- If select=1 and r/w=0, ???



 
## Basic (NOR) S – R Latch

- Cross-coupling two NOR gates gives the S – R Latch:
- Which has the time sequence



behavior:

 
**S = 1, R = 1 is forbidden as input pattern**



Time	R	S	Q	$\bar{Q}$	Comment
	0	0	?	?	Stored state unknown
	0	1	1	0	"Set" Q to 1
	0	0	1	0	Now Q "remembers" 1
	1	0	0	1	"Reset" Q to 0
	0	0	0	1	Now Q "remembers" 0
	1	1	0	0	forbidden
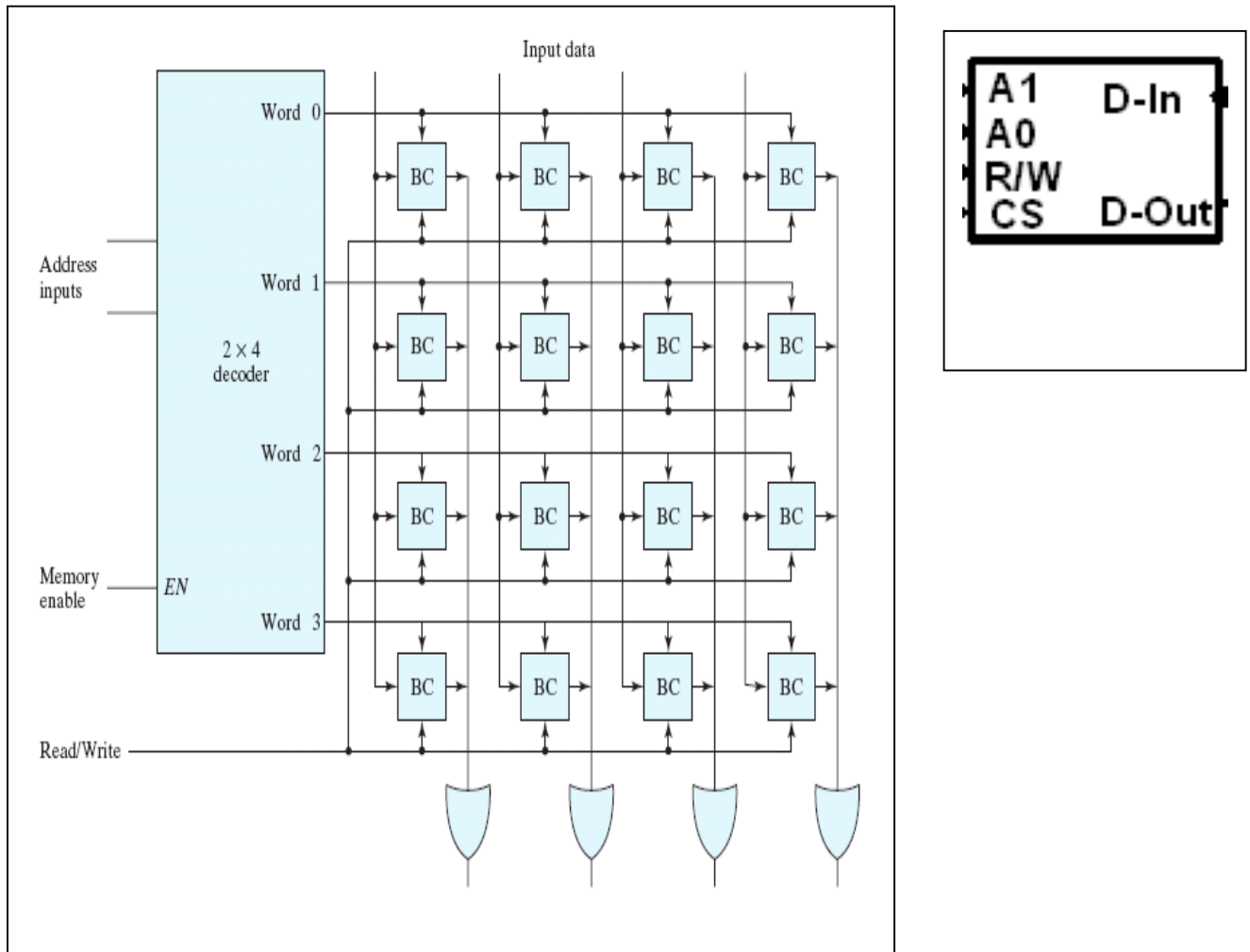
## BUILDING A 4x4 RAM


Decoder : decodes the n address lines to  $2^n$  word select lines




 
## Decoder


- Decoder – converts  $n$ -bit input lines to a maximum of  $2^n$  unique output lines



- $n$ -to- $m$  line decoders, where  $n \leq m \leq 2^n$
- Function: generate  $2^n$  (or fewer) minterms for the  $n$  input variables
- 2-to-4-Line Decoder
- Each line  $D_i$  is a minterm

$A_1$	$A_0$	$D_0$	$D_1$	$D_2$	$D_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

(a)

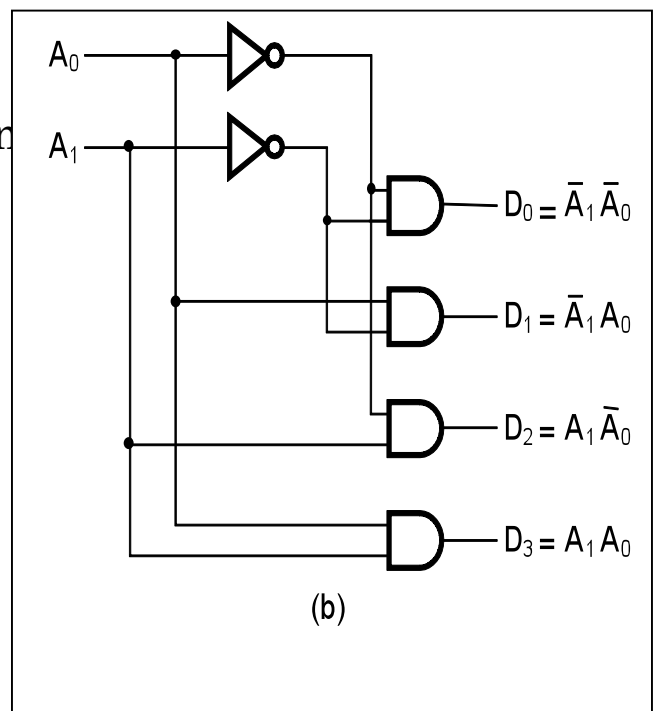


(b)

## Decoder Examples


### 3-to-8-Line Decoder

Inputs			Outputs							
<i>x</i>	<i>y</i>	<i>z</i>	<i>D</i> <sub>0</sub>	<i>D</i> <sub>1</sub>	<i>D</i> <sub>2</sub>	<i>D</i> <sub>3</sub>	<i>D</i> <sub>4</sub>	<i>D</i> <sub>5</sub>	<i>D</i> <sub>6</sub>	<i>D</i> <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

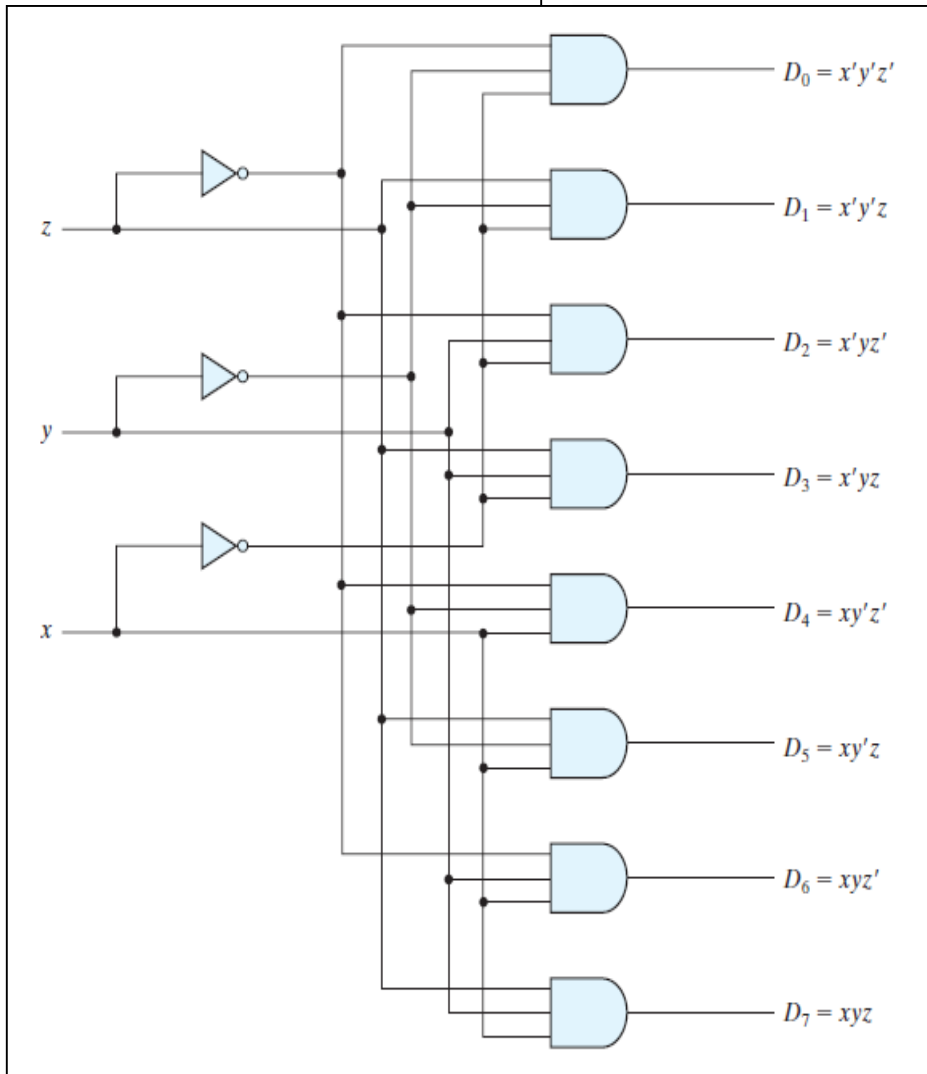
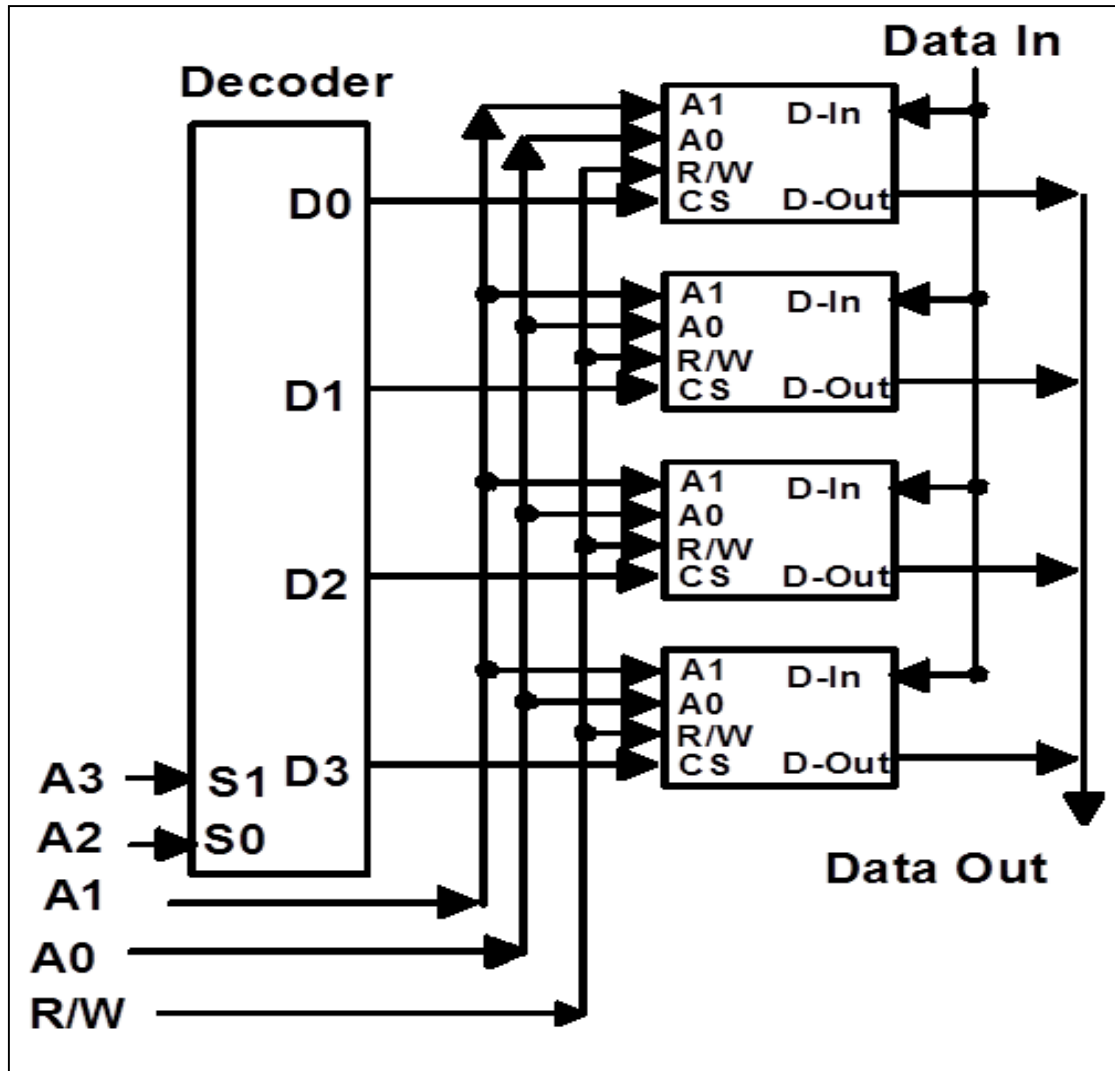
## Making Larger Memories


- To make larger memories from smaller ones, we tie all address, data, and R/W lines in parallel, and using the decoded higher order address bits to control CS.



- Using the 4x1 memory chips to construct a 16x1 memory.
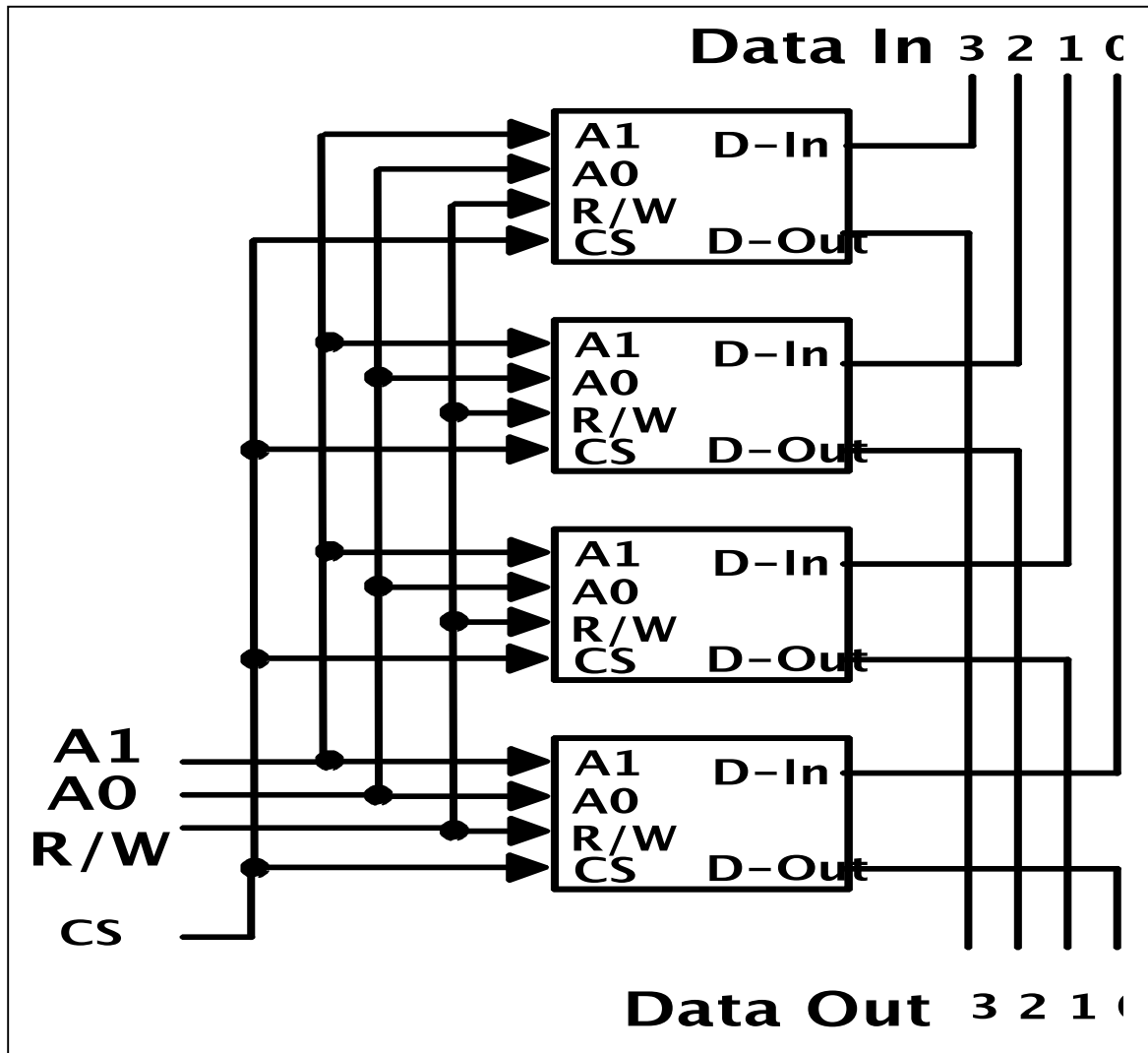
## Making Wider Memories

- To construct wider memories from narrow ones, we tie the address and control lines in parallel and keep the data lines separate.



- Using the 4x1 memory chips to build a 4x4 memory.

## Making larger memories

- Make a 256kx8 memory from 64kx8 memory chips.
  - How many chips?
  - What decoder?
  - How to arrange address lines, data lines, and read/write control?

## Making Wider Memories


- Make a 64Kx16 memory from 64Kx8 memory chips.
  - How many chips?
  - What decoder?
  - How to arrange address lines, data lines, and read/write control?

## Making Wider and Larger Memory

- Make a 256Kx16 memory from 64Kx8 memory chips.
  - How many chips?
  - What decoder?
  - How to arrange address lines, data lines, and read/write control?

## Coincident Decoding

 - Problem of a single decoder
  - For 1Kx1 memory, a huge  $10\text{-}2^{10}$  decoder is needed
- Solution: coincident decoding
  - Two  $5\text{-}2^5$  decoders are used.
  - One decoder decodes higher bits in address lines.
  - The other decodes lower bits in address lines.
  - Memory units are arranged in an array.
  - A memory unit is selected if both decoders select it.




## Coincident Decoding

- Given the 1Kx4 memory with coincident decoding.
  - X takes the higher 5 bits of an address
  - Y takes the lower 5 bits of an address
- Write 1011 to address 0110000010
  - X=?
  - Y=?
  -

Read from address 0000110100

## ROM

Similar to RAM, but no data input lines.

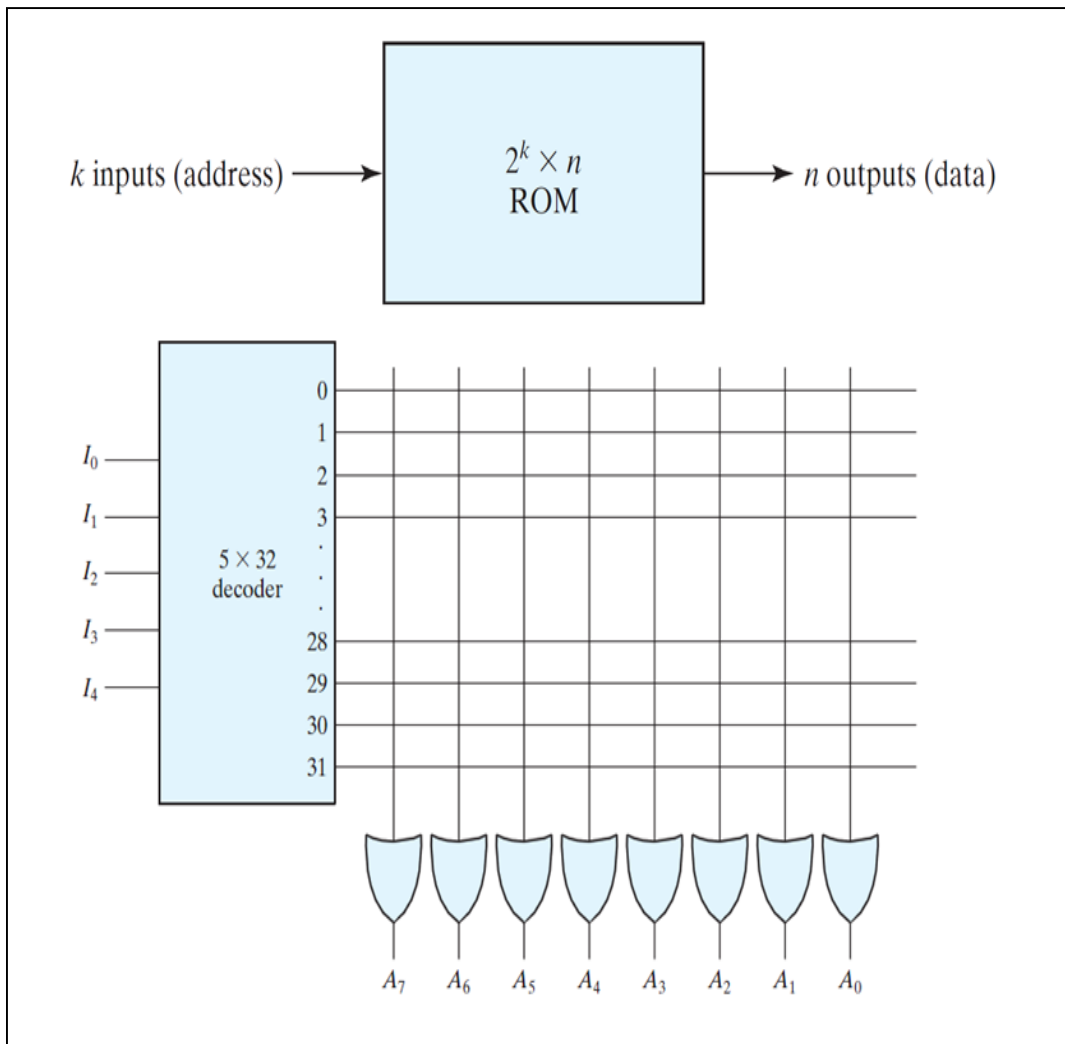




- Stored information in a ROM is represented by a truth table.

**Table 7.3**  
*ROM Truth Table (Partial)*


Inputs					Outputs							
$I_4$	$I_3$	$I_2$	$I_1$	$I_0$	$A_7$	$A_6$	$A_5$	$A_4$	$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		⋮							⋮			
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

 - 1 (x) means a connection; 0 means no connection.
- Each gate is a OR gate with inputs from all addresses.


 
# ROM

- What data is at address
- 0 : 10110110
- 1 : 00011101
- 2
- 3
- 28
- 29
- 30
- 31




## Applications of ROM

- Design a circuit to take a 3-bit number and output its square.

*Truth Table for Circuit of Example 7.1*

Inputs			Outputs						Decimal
$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$	$B_1$	$B_0$	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

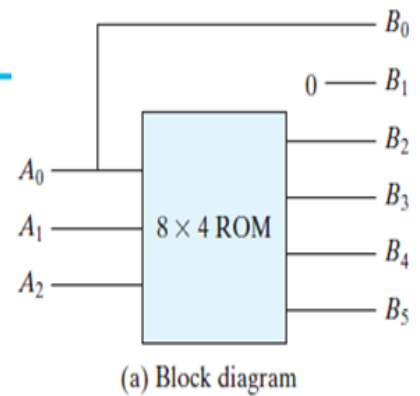

## Types of ROM

- **MROM : Mask programming ROM**
  - Programmed when being manufactured
- **PROM : Programmable ROM**
  - Fuses intact when being manufactured
  - Allow programming once, irreversible
- **EPROM : Erasable PROM**
  - Erase with special ultraviolet, and then reprogram
- **EEPROM : Electronically EPROM**
  - Erase with special charge, and then reprogram