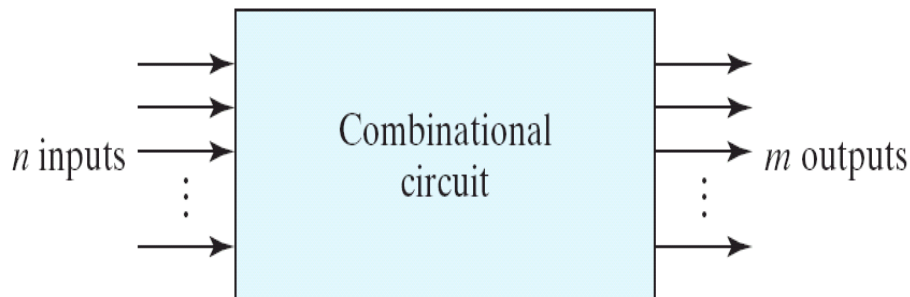


Outline

- Analysis of Combinational Logic (CL)
- Design of CL
- Classical CL circuits
- Adder

Combinational Logic (CL)

- CL consists of input variables, logic gates, and output variables.
- CL is a logic that has no feedback path from output to input and no memory elements.




- For n input variable, 2^n binary input combinations.
- Specified with a truth table, list output values for each combination of input variables.
- Described by m Boolean functions

COMBINATIONAL LOGIC (CL)

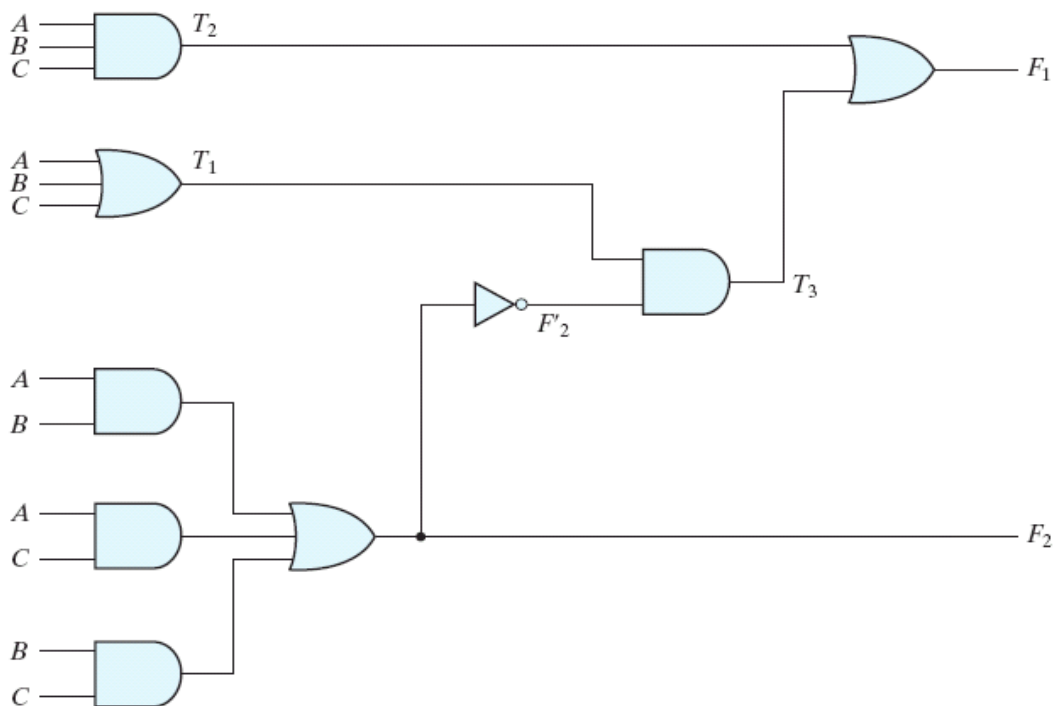- Tasks:
 - (1) **Analysis of CL:** Analyze the behavior of a given logic circuit
 - (2) **Design of CL:** Synthesize a circuit that will have a given behavior

Analysis of CL

- Analysis steps
 - Given a CL circuit
 - Obtain a function for each output
 - Derive a truth table for each output
 - Interpret the operation



Analysis of CL

- $F_2 = AB + AC + BC$
- $F_1 = A'BC' + A'B'C + AB'C' + ABC$
- Interpretation

A	B	C	F₂	F₁
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Design of CL

- Design steps
 - Given the specification of a circuit
 - Determine the inputs and the outputs
 - Derive a truth table for each output
 - Obtain a function for each output
 - Draw the circuit
- Code Conversion
 - BCD to Excess-3

Four Different Binary Codes for the Decimal Digits

Decimal Digit	BCD 8421	2421	Excess-3	8, 4, -2, -1
0	0000	0000	0011	0000
1	0001	0001	0100	0111
2	0010	0010	0101	0110
3	0011	0011	0110	0101
4	0100	0100	0111	0100
5	0101	1011	1000	1011
6	0110	1100	1001	1010
7	0111	1101	1010	1001
8	1000	1110	1011	1000
9	1001	1111	1100	1111
<hr/>				
	1010	0101	0000	0001
Unused	1011	0110	0001	0010
bit	1100	0111	0010	0011
combi-	1101	1000	1101	1100
nations	1110	1001	1110	1101
	1111	1010	1111	1110

Design of CL

- Code Conversion
 - BCD to Excess-3

Design steps

- Given the specification of a circuit
- Determine the inputs and the outputs
- Derive a truth table for each output
- Obtain a function for each output
- Draw the circuit

Truth Table for Code-Conversion Example

Input BCD				Output Excess-3 Code			
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

Design of CL

K-map


- $w = A+BC+BD$
- $x = B'C+B'D+BC'D'$
- $y = CD+C'D'$
- $z = D'$

Design steps

- Given the specification of a circuit
- Determine the inputs and the outputs
- Derive a truth table for each output
- Obtain a function for each output
- Draw the circuit

Multi-level

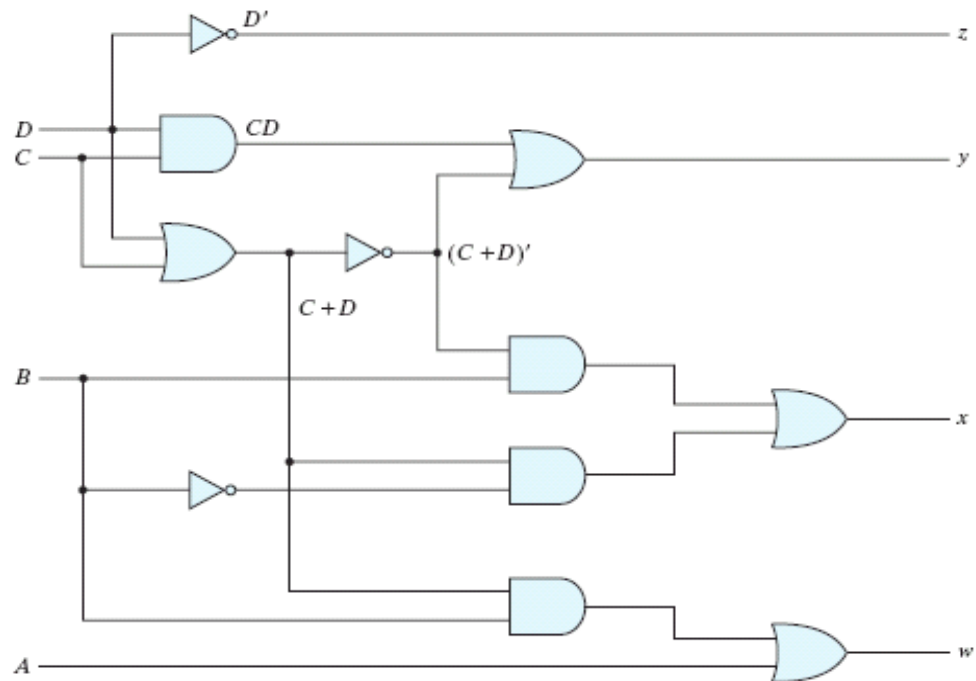- $w = A+B(C+D)$
- $x = B'(C+D)+B(C+D)'$
- $y = CD+(C+D)'$
- $z = D'$




Design of CL

- Build a circuit to display a decimal digit(BCD) in a 7-segment component.

Design steps

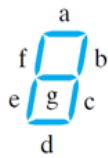- Given the specification of a circuit
- Determine the inputs and the outputs
- Derive a truth table for each output
- Obtain a function for each output
- Draw the circuit



(a) Segment designation



(b) Numeric designation for display

BCD Input				Seven-Segment Decoder						
A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
All other inputs				0	0	0	0	0	0	0

$$a = A'C + A'BD + A'B'D' + AB'C'$$

$$b = ?$$

$$c = ?$$

..

..

..

$$g = ?$$

Outline



- Analysis of Combinational Logic (CL)
- Design of CL
- Classical CL circuits
- Adder

Half Adder

- Addition of two binary bits
- $x+y = ?$
 - $S = x'y + xy' = x \oplus y$
 - $C = xy$

Half Adder

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

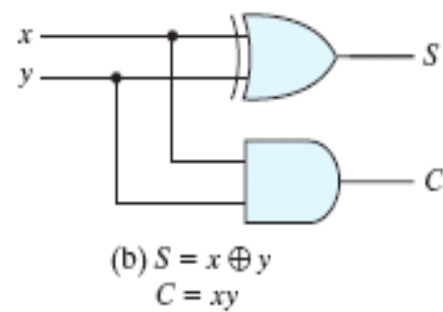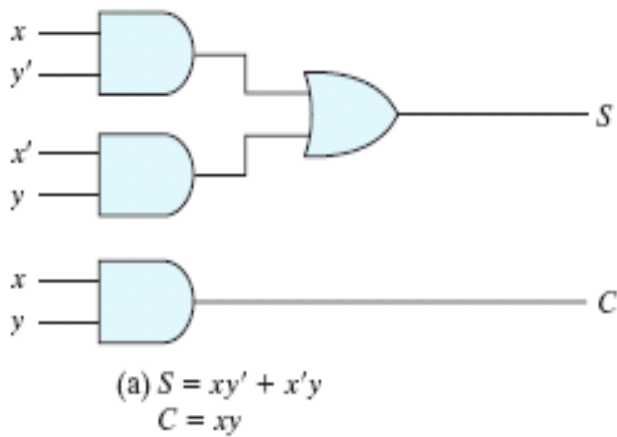

Full Adder

- Addition of three bits (two significant bits and a previous carry)
- $x+y+z = ?$

Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Full Adder

Adds three bits (two significant bits and a previous carry)

- Note that the Sum alternates between an XOR and XNOR depending upon $Carry_{in}$
- Note that the $Carry_{out}$ alternates between an AND and an OR depending upon $Carry_{in}$

- $S = x'y'z + x'yz' + xy'z' + xyz$
- $C = xy + xz + yz$


$Carry_{in}$	X	Y	Sum	$Carry_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

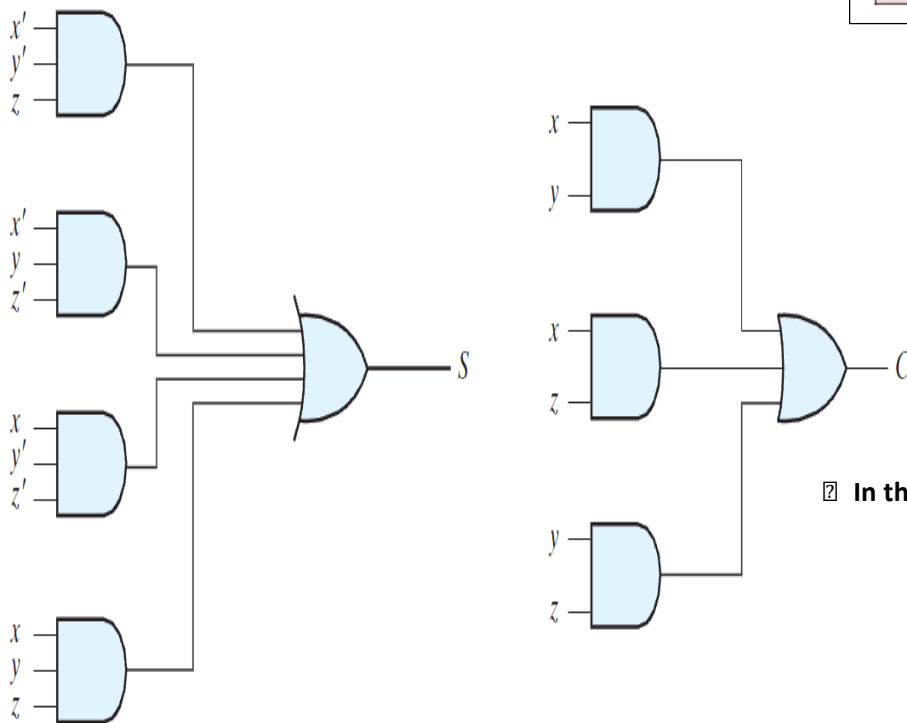

☐ In this figure, Z = $Carry_{in}$ and C = $Carry_{out}$

Full Adder

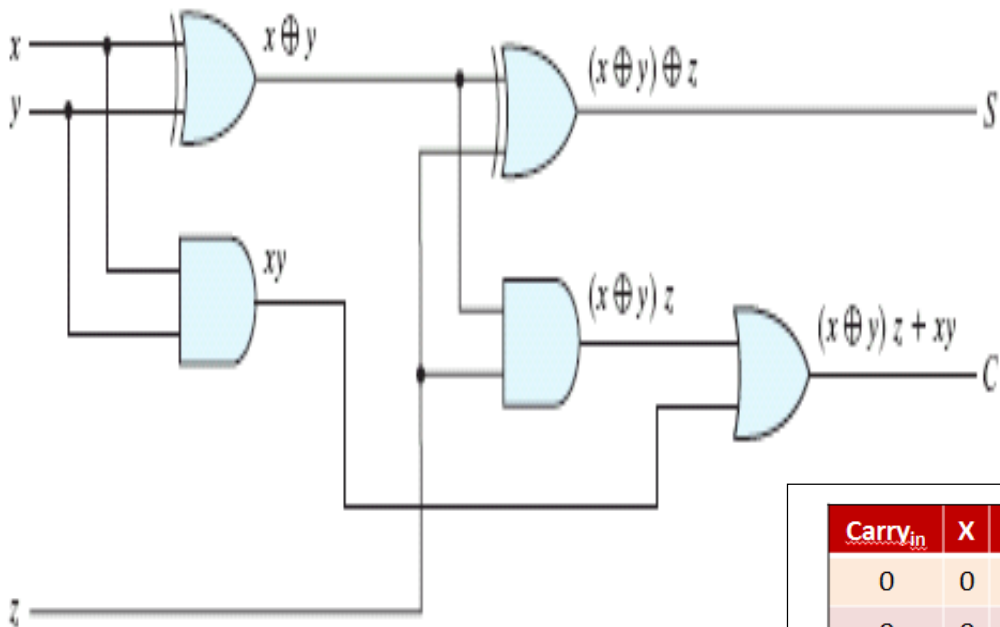- Implemented with half adder ?
- $S = x'y'z + x'yz' + xy'z' + xyz = z \oplus (x \oplus y)$
- $C = xy + xz + yz = z(xy' + x'y) + xy$



Recall: For a half-adder:

$$S = X'Y + XY' = X \oplus Y$$

$$C_{in} = XY$$

$$C_{out} = XY + XC_{in} + YC_{in}$$

$$= XY(C_{in} + C_{in}') + XC_{in}(Y + Y') + YC_{in}(Z + Z')$$

$$= C_{in}(X \oplus Y) + XY$$

For a Full-adder:

$$S = X'Y'C_{in} + X'YC_{in}' + XY'C_{in}' + XYC_{in}$$

$$= (X'Y' + XY)C_{in} + (X'Y + XY')C_{in}'$$


$$= (X'Y' + XY)C_{in} + (X \oplus Y)C_{in}'$$

$$= (X \oplus Y) \oplus C_{in}$$

Carry _{in}	X	Y	Sum	Carry _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Binary Adder

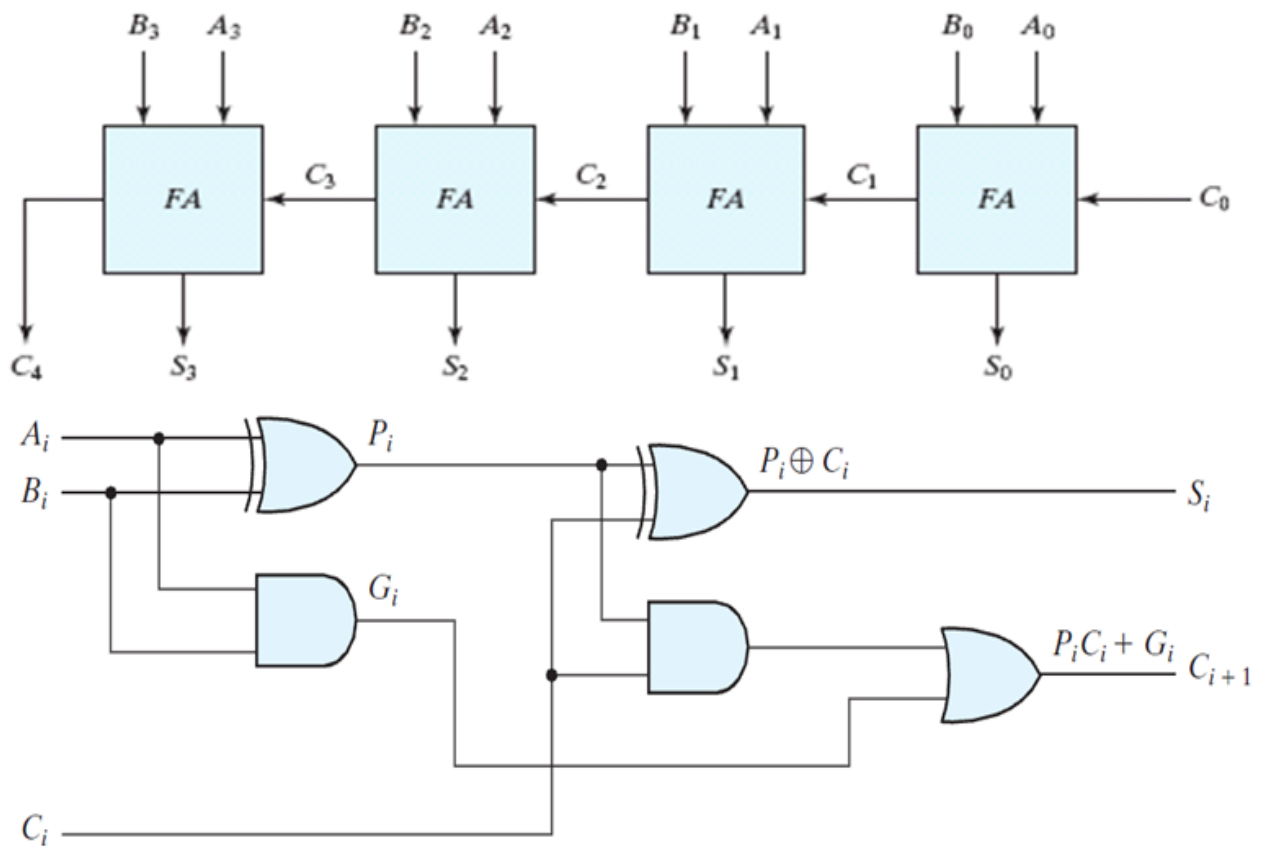- Arithmetic sum of two binary numbers
- A chain of full adders : ripple (serial) adder



Application of Adder

- Binary multiplier
 - $B_3B_2B_1B_0 \times A_2A_1A_0$

